Code:


```
module Assignment_3(
input wire A,
input wire [1:0]S,
output wire T0,T1,T2,T3
);
  assign T0=(S==2'b00)?A:0;
  assign T1=(S==2'b01)?A:0;
  assign T2=(S==2'b10)?A:0;
  assign T3=(S==2'b11)?A:0;
endmodule
Test Bench code:
module Assignment_3_tb();
reg A;
reg [1:0]S;
wire T0,T1,T2,T3;
Assignment_3 uut (
  .A(A),
  .S(S),
  .T0(T0),
  .T1(T1),
  .T2(T2),
  .T3(T3)
);
  initial begin;
    A=1;S=2'b00; #10;
    A=1;S=2'b01; #10;
    A=1;S=2'b10; #10;
    A=1;S=2'b11; #10;
    A=1;S=2'bX;#10;
```

```
A=1;S=2'bZ;#10;
```

\$stop();

end

endmodule

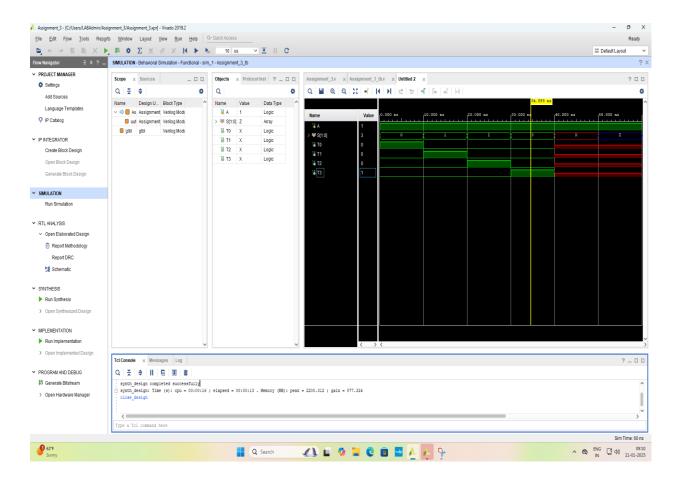

2)

Code:

module assignment_3(

input A,

input B,

input Cin,

output Sum,

output Cout

);

```
wire n1,n2,n3,n4,n5,n6,n7,n8;
nand (n1,A,B);
nand (n2,A,n1);
nand (n3,B,n1);
wire N;
             //AxorB
nand (N,n2,n3);
nand (n4,N,Cin);
nand (n5,N,n4);
nand (n6,Cin,n4);
nand (Sum,n5,n6);
nand (n7,A,B);
nand (n8,N,Cin);
nand (Cout,n7,n8);
endmodule
Test Bench Code:
module assignment_3_tb();
reg A,B,Cin;
wire Sum, Cout;
assignment_3 uut(
  .A(A),
  .B(B),
  .Cin(Cin),
```

```
.Sum(Sum),
  .Cout(Cout)
);
 initial begin
  A=0;B=0;Cin=0;#10;
  A=0;B=0;Cin=1;#10;
  A=0;B=1;Cin=0;#10;
  A=0;B=1;Cin=1;#10;
  A=1;B=0;Cin=0;#10;
  A=1;B=0;Cin=1;#10;
  A=1;B=1;Cin=0;#10;
  A=1;B=1;Cin=1;#10;
  A=1'bx;B=0;Cin=0;#10;
  A=1'bx;B=1;Cin=0;#10;
  A=1'bz;B=0;Cin=0;#10;
  A=1'bz;B=1;Cin=0;#10;
end
```

endmodule

